

Date 17 or wednesday
2023

(sixth class) Pg # 19

ADDERS:-

A digital circuit used for addition of numbers. There are 2 types of adders

- Half Adder.
- Full Adder.


1) HALF ADDER:-

→ Add two bits

*) Produces a sum & carry

→ PROBLEM:- Can not use it to build larger inputs.
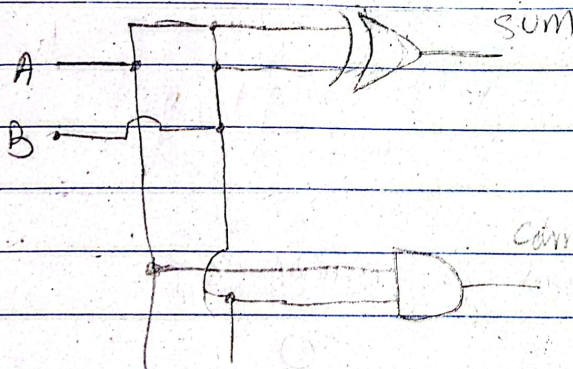
$$\rightarrow \boxed{\text{Sum} = A \cdot B + A \cdot B'}$$




TRUTHTABLE (2nd)

TRUTHTABLE (1st)

A	B	C (COP)	A	B	Sum	CARRY (COP)
0	0	0	0	0	0	0
0	1	1	0	1	1	0
1	0	1	1	0	1	0
1	1	1	1	1	0	1

BY BLOCK DIAGRAM

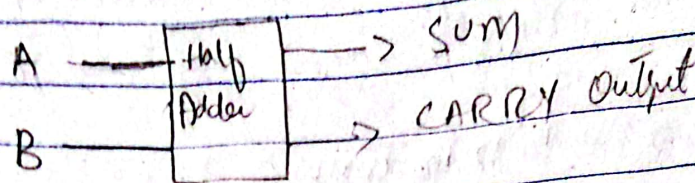

2) FULL ADDER

→ Adds three 1-bit values to like half adder, produces a sum & carry


→ SIMPLE TECHNIQUE :-

(*) Connect "Cout" of an adder to the next.

(*) This is known as "Ripple Carry Adder".

REPRESENTATION

i) BY BLOCK DIAGRAM

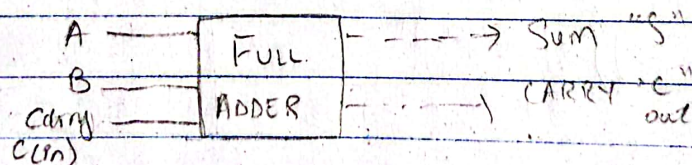

ii) BY TRUTH-TABLE

A	B	CARRY "C" IN	SUM "S" O/P	CARRY "C" O/P
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

4.21
10
4

pg# 21

iii) BY GRAPHICAL REPRESENTATION

